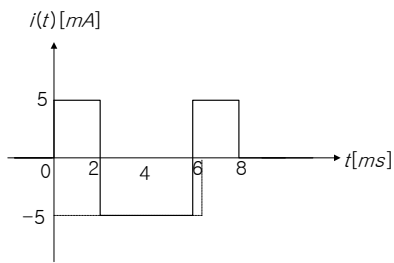



IT@CookBook


## 예제로 배우는 회로이론

### 연습문제 정답

# Chapter 01

번호	답
1.1	(a) $\lambda = 3[\text{mm}]$ (b) $a = 100[\text{km/s}]$ (c) $l = 100[\mu\text{m}]$ (d) $W = 100[\mu\text{W}]$
1.2	(a) $Q = 1.6[\text{nC}]$ (b) $Q = 0.8[\text{mC}]$ (c) $Q = 3.2[\text{MC}]$ (d) $Q = 0.16[\text{TC}]$
1.3	(a) $N = 6.25 \times 10^{18}[\text{개}]$ (b) $N = 6.25 \times 10^{15}[\text{개}]$ (c) $N = 6.25 \times 10^{12}[\text{개}]$ (d) $N = 6.25 \times 10^{10}[\text{개}]$
1.4	(a) $i(t) = -3 \times 10^3 \sin 10^3 t [\text{A}]$ (b) $i(t) = -100e^{-10t} [\text{mA}]$ (c) $i(t) = 5[\mu\text{A}]$
1.5	
1.6	(a) $q(t) = 5t + 100 [\text{mC}]$ (b) $q(t) = 3 \sin 10^3 t [\mu\text{C}]$ (c) $q(t) = 5e^{-10t} - 3 [\text{C}]$
1.7	<p>(a) <math>t &lt; 0: i(t) = 0</math>, <math>0 \leq t \leq 5\text{ms}: i(t) = t[\text{A}]</math>, <math>5\text{ms} \leq t \leq 9\text{ms}: i(t) = 5[\text{mA}]</math>  <math>9\text{ms} \leq t \leq 14\text{ms}: i(t) = -10^3 t + 14[\text{mA}]</math>, <math>t \geq 14\text{ms}: i(t) = 0</math></p> <p>(b) <math>t &lt; 0: q(t) = 0</math>, <math>0 \leq t \leq 5\text{ms}: i(t) = \int_0^t t dt + q(0) = \frac{1}{2}t^2 [\text{C}]</math>, <math>q(5\text{ms}) = 12.5[\mu\text{C}]</math>,  <math>5\text{ms} \leq t \leq 9\text{ms}: q(t) = \int_{5\text{ms}}^t 5 \times 10^{-3} dt + q(5\text{ms}) = 5 \times 10^{-3} t + 1.25 \times 10^{-5}</math>  <math>\therefore q(t) = 5 \times 10^3 t + 12.5[\mu\text{C}]</math>, <math>q(9\text{ms}) = 57.5[\mu\text{C}]</math></p>

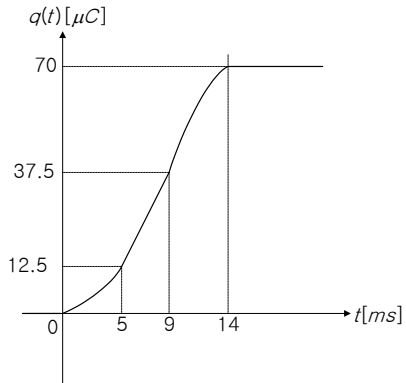	$9ms \leq t \leq 14ms : q(t) = \int_{9ms}^t \{-t + 14 \times 10^{-3}\} dt + q(9ms)$ $\therefore q(t) = -\frac{1}{2}t^2 + 14 \times 10^{-3}t - 28[\mu C], q(14ms) = 70[\mu C]$ $t \geq 14ms : q(t) = 70[\mu C]$ <p>(c)</p> 
<b>1.8</b>	<p>(a) <math>v_{ab} = -0.1[V]</math></p> <p>(b) <math>v_{ab} = 1.0[V]</math></p> <p>(c) <math>v_{ab} = 1.4[V]</math></p>
<b>1.9</b>	<p>(a) <math>p_1 = 150[W]</math></p> <p>(b) <math>p_2 = 50[W]</math></p> <p>(c) <math>p_3 = 60[W]</math></p> <p>(d) <math>p_4 = 50[W]</math></p> <p>(e) <math>p_5 = 10[W]</math></p>
<b>1.10</b>	<p>(a) <math>p_1 = 50[W]</math></p> <p>(b) <math>p_2 = 7[W]</math></p> <p>(c) <math>p_3 = 8[W]</math></p> <p>(d) <math>p_4 = 9[W]</math></p> <p>(e) <math>p_5 = 10[W]</math></p> <p>(f) <math>p_5 = 16[W]</math></p>
<b>1.11</b>	<p>(a) <math>W = 1.8[MJ]</math></p> <p>(b) <math>W = 1.44[MJ]</math></p> <p>(c) <math>W = 9.6[MJ]</math></p>

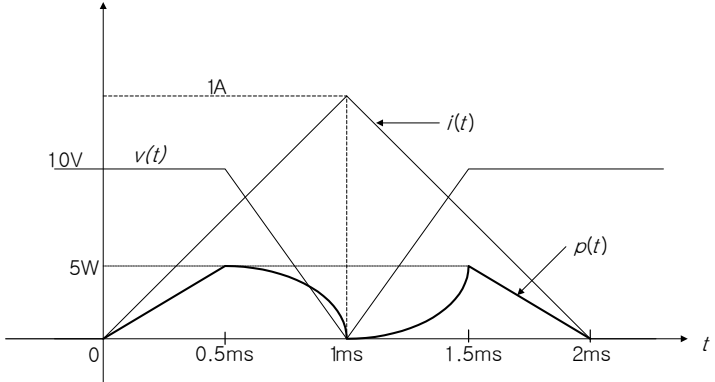1.12	
1.13	<p>(a) <math>V = 5I</math></p> <p>(b) <math>V = -10I</math></p> <p>(c) <math>V = 5I - 10</math></p> <p>(d) <math>V = 10I + 10</math></p>
1.14	<p>(a) <math>i = 3i_x</math></p> <p>(b) <math>v_6 = 6i_x</math></p> <p>(c) <math>v_2 = 2i</math></p> <p>(d) <math>v = 4i</math></p>
1.15	$V_o = -197/2 [\text{V}]$
1.16	$P = 80 [\text{W}]$
1.17	$R = 2.5 [\Omega]$
1.18	240 W 증가함
1.19	<p>(a) <math>R_{100m} = 35 [\text{V}]</math></p> <p>(b) <math>P = 2 [\text{W}]</math></p> <p>(c) <math>R = 6.37 (\Omega \text{cm})^{-1}</math></p>

## Chapter 02

번호	답
2.1	(a) $I = 4[\text{A}]$ (b) $P = 80[\text{W}]$
2.2	$P = \frac{2420}{3}[\text{W}]$
2.3	$R_1 = 4[\Omega]$ , $R_2 = 10[\Omega]$ , $I_1 = 1[\text{A}]$ , $V_1 = 6\text{V}$ , $V_2 = 4\text{V}$
2.4	$I_2 = 2[\text{A}]$ , $I_3 = 1[\text{A}]$ , $I_4 = 3[\text{A}]$ , $I_1 = 6[\text{A}]$
2.5	(a) $v_x = 4[\text{V}]$ , $V_s = 1[\text{V}]$ , $i_x = 0.5[\text{A}]$ (b) $P = 5[\text{W}]$
2.6	$V_1 = 20[\text{V}]$ $V_2 = 40[\text{V}]$
2.7	(a) $V_1 : V_2 = 1 : -2$ (b) $I_1 = 2[\text{A}]$ (c) $P = 40[\text{W}]$ (d) $P = 16[\text{W}]$
2.8	$V_o = 4[\text{V}]$ $P = 12[\text{W}]$
2.9	$V_o = -4[\text{V}]$ $P = -8[\text{W}]$
2.10	$V_1 = 6[\text{V}]$ $V_2 = 4[\text{V}]$
2.11	$V = 18[\text{V}]$ $I_o = 0.4[\text{mA}]$
2.12	$I_o = \frac{4}{9}[\text{mA}]$ $V_o = \frac{8}{3}[\text{V}]$
2.13	$I_o = -\frac{1}{3}[\text{A}]$
2.14	$I_s = \frac{5}{3}[\text{mA}]$ $V_o = \frac{40}{9}[\text{V}]$
2.15	$V_s = 30[\text{V}]$ $I_o = 3[\text{A}]$
2.16	$V_o = \frac{20}{3}[\text{V}]$
2.17	(a) $R_{eq} = R$ (b) $R_{eq} = R$ (c) $R_{eq} = R$ (d) $R_{eq} = \frac{3}{5}R$
2.18	$R_{eq} = 3.6[\Omega]$
2.19	$R_{ab} = \frac{83}{6}\Omega$
2.20	$I_s = \frac{32}{109}[\text{A}]$
2.21	(a) $P_t = 240[\text{W}]$ (b) $P_t = 15[\text{W}]$

<b>2.22</b>	$R_{eq} = 20[\Omega]$
<b>2.23</b>	(a) $R_{ab} = 11.6[\Omega]$ (b) $R_{eq} = 5[\Omega]$
<b>2.24</b>	$V_o = 0.25[V]$
<b>2.25</b>	$R_{eq} = 10[\Omega]$
<b>2.26</b>	$P_{BOX} = \frac{500}{3}[W]$
<b>2.27</b>	(a) $V = 2I + 13/3$ (b) $V = 10I + 5$
<b>2.28</b>	(a) $V = 4I$ (b) $I = 3i_o + 18$
<b>2.29</b>	$V = 7I$





## Chapter 03







번호	답
3.1	$V_o = 2[\text{V}]$
3.2	$V_o = 6[\text{V}]$
3.3	$i_o = 5\text{A}$
3.4	$v_x = 10[\text{V}]$
3.5	$v_x = 2[\text{V}]$
3.6	$v_x = 0$
3.7	$v_x = 1[\text{V}]$
3.8	$v_x = 0, v_y = -7.5[\text{V}]$
3.9	$i_o = 3[\text{A}]$
3.10	$v_x = 2[\text{V}], i_o = 0$
3.11	$V_o = 4[\text{V}]$
3.12	$i_o = 1[\text{A}]$
3.13	$V_x = 2[\text{V}]$
3.14	$i_o = 1.5[\text{A}]$
3.15	$i_x = 2[\text{A}]$
3.16	$v_o = -2[\text{V}]$
3.17	$v_x = 5[\text{V}]$
3.18	$v_o = 10[\text{V}]$
3.19	$V_x = -6[\text{V}], i_o = 2[\text{A}]$
3.20	$I_o = 1[\text{A}], V_x = 4[\text{V}]$
3.21	$I_o = 1[\text{A}]$



<b>3.22</b>	$V_o = 2[\text{V}]$
<b>3.23</b>	$P_{R_L} = 5[\text{W}]$
<b>3.24</b>	$V_x = 4[\text{V}]$
<b>3.25</b>	$i_x = \frac{41}{42}[\text{A}]$
<b>3.26</b>	$V_o = 10[\text{V}]$
<b>3.27</b>	$P_{1A} = 2[\text{W}]$

## Chapter 04

번호	답
4.1	(a) $v_s = 40[\text{V}]$ (b) $i = 0.25[\text{A}]$
4.2	(a) $v_s = 45[\text{V}]$ (b) $v_o = \frac{10}{9}[\text{V}]$
4.3	(a) $v_o = 10[\text{V}]$ (b) $i_s = 1[\text{A}]$ (c) $v_o = 14[\text{V}]$
4.4	$V_o = 2[\text{V}]$
4.5	$V_x = -2[\text{V}]$
4.6	$I_1 = -1[\text{A}]$
4.7	$P_{\frac{3}{8}\Omega} = -42[\text{W}]$
4.8	(a) $v_o = 12[\text{V}]$ (b) $P_{2\Omega} = 72[\text{W}]$
4.9	$V_x = -24[\text{V}]$
4.10	$V_o = \frac{1}{3} \left( \frac{V_1}{8} + \frac{V_2}{4} + \frac{V_3}{2} \right)$
4.11	$V = 10I + 10$
4.12	$I = \frac{V}{4} - 2.5$ 혹은 $V = 4I + 10$
4.13	$V = 7I + 12$
4.14	$v = 8i + 32$
4.15	$v_x = 1\text{V}$
4.16	$V_o = \frac{1}{3} \left( \frac{V_1}{8} + \frac{V_2}{4} + \frac{V_3}{2} \right)$
4.17	(a) $v = 10i + 100$ (b) $V_{OC} = 100[\text{V}], R_{TH} = 10[\Omega]$

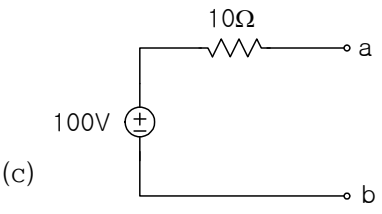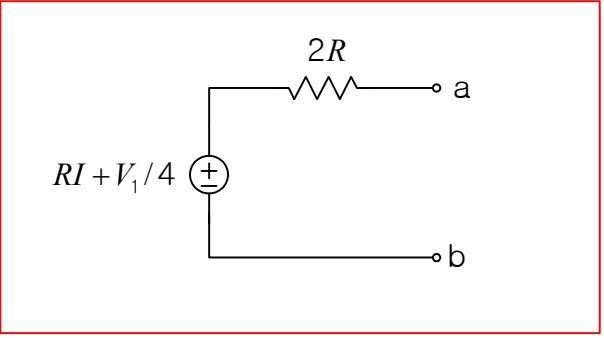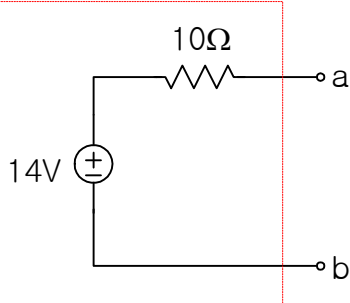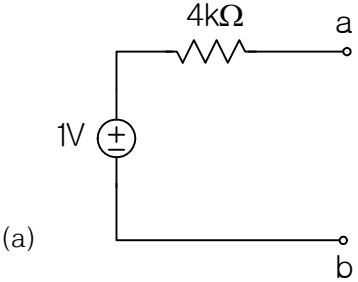	 <p>(c)</p>
4.18	
4.19	$V_s = 12[\text{V}]$
4.20	
4.21	 <p>(a)</p> <p>(b) <math>v_o = 0.5[\text{V}]</math></p>
4.22	(a) $V = 10 \cdot I + 3, I = 0.1 \text{ V} - 0.3$

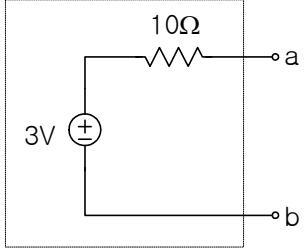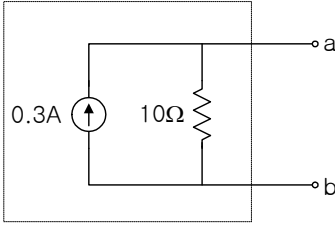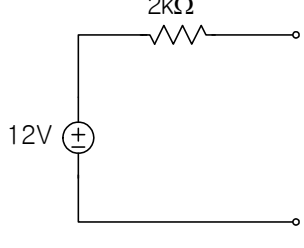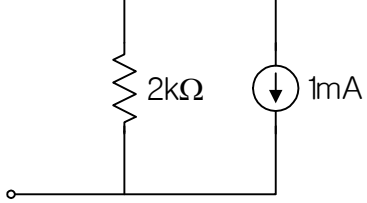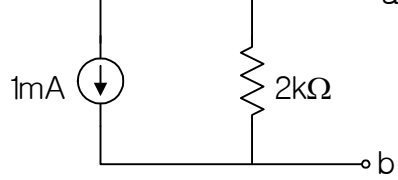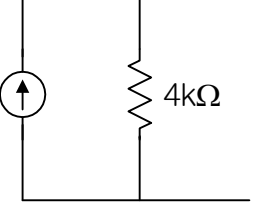
	<div style="display: flex; flex-direction: column; align-items: center;"> <div style="margin-bottom: 20px;"> <p>(b)</p>  </div> <div> <p>(c)</p>  </div> </div>
<b>4.23</b>	<div style="display: flex; flex-direction: column; align-items: center;"> <div style="margin-bottom: 20px;"> <p>(a)</p>  </div> <div> <p>(b)</p>  </div> <div style="margin-top: 20px;"> <p>(c) <math>v_o = 4.2[\text{V}]</math></p> </div> </div>
<b>4.24</b>	<div style="display: flex; flex-direction: column; align-items: center;"> <div style="margin-bottom: 20px;"> <p>(a) <math>i_{SC} = -1[\text{mA}]</math>, <math>R_{TH} = 2[\text{k}\Omega]</math></p> </div> <div style="margin-bottom: 20px;"> <p>(b) <math>i_{SC} = -1[\text{mA}]</math>, <math>R_{TH} = 2[\text{k}\Omega]</math></p> </div> <div> <p>(c)</p>  </div> </div>
<b>4.25</b>	<p><math>I_o = \frac{10}{7}[\text{A}]</math></p>
<b>4.26</b>	<p>(a)</p> 

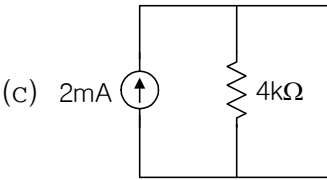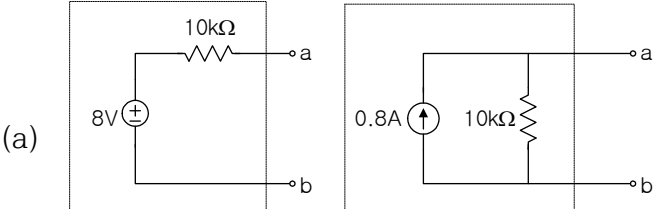	<p>(b) <math>\therefore I = \frac{V}{4k\Omega} = 2[\text{mA}]</math></p> <p>(c) </p>
<b>4.27</b>	<p>(a) </p> <p style="text-align: center;">테브난 등가회로                      노턴의 등가회로</p> <p>(b) <math>v_o = 3[\text{V}]</math></p>
<b>4.28</b>	$P_{\max} = 10[\text{mW}]$
<b>4.29</b>	$V_s = -75[\text{V}]$ or $105[\text{V}]$
<b>4.30</b>	$R_L = 20[\Omega]$ , $P_{\max} = 20[\text{W}]$
<b>4.31</b>	$R_L = 3[\Omega]$ , $P_{\max} = \frac{4}{3}[\text{W}]$
<b>4.32</b>	$R_L = 4[\Omega]$ , $P_{\max} = \frac{(10\text{V})^2}{4\Omega} = 25[\text{W}]$
<b>4.33</b>	$R_L = 4[\Omega]$ , $P_{4\Omega} = 1[\text{W}]$
<b>4.34</b>	$R_L = 10[\Omega]$ , $P_{\max} = 0.1[\text{W}]$
<b>4.35</b>	$R_L = 3[\Omega]$ , $P_{\max} = \frac{25}{12}[\text{W}]$


## Chapter 05

번호	답
5.1	$\frac{v_o}{v_i} = \frac{10^{-2} + 10^8}{10^{-2} + 10^3 + 10^8} \simeq 1$
5.2	(a) $\frac{v_o}{v_i} = 1$ (b) $\frac{v_o}{v_i} = \frac{10^{-2} + 10^8}{10^{-2} + 10^3 + 10^8} \simeq 1$
5.3	$I_o = 1.6[\text{mA}]$
5.4	$I_o = -8[\text{mA}], V_o = -15[\text{V}]$
5.5	$V_o = -2.5[\text{V}]$
5.6	$v_o/v_i = -3$
5.7	$V_o = -8V_i$
5.8	$v_o = \left(1 + \frac{R_4}{R_3}\right) \cdot \left(\frac{R_1 \cdot R_2}{R_1 + R_2}\right) \cdot \left(\frac{v_1}{R_1} + \frac{v_2}{R_2}\right)$
5.9	$I_o = 4.6[\text{mA}]$
5.10	$i_o = -1.6[\text{mA}]$
5.11	$v_o = -5v_1 + \frac{13}{4}v_2$
5.12	$V_o = 10[\text{V}]$
5.13	$i_o = 1.2[\text{mA}], v_o = 10[\text{V}]$
5.14	$v_o = -3v_1 + \frac{5}{2}v_2$
5.15	$v_o = -a(v_1 + v_2) + (a + 1/2)(v_3 + v_4)$
5.16	<p>(a)</p>


(b)

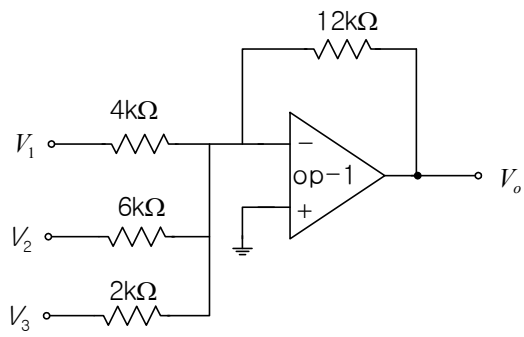

(c)

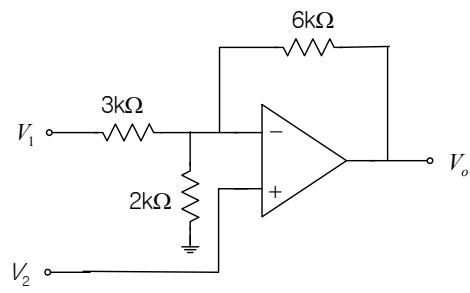

(d)

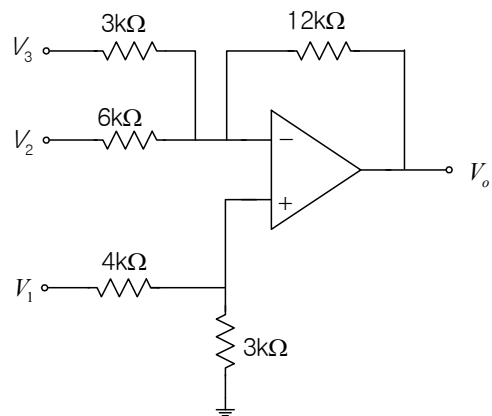

	<p>(e)</p> <p>The circuit diagram shows an operational amplifier (op-amp) configured with multiple inputs and feedback. The non-inverting input (+) is connected to a network of resistors: a 30kΩ resistor from input <math>V_2</math>, a 10kΩ resistor from input <math>V_1</math>, and a 6kΩ resistor connected to ground. The inverting input (-) is connected to a network of resistors: a 5kΩ resistor from input <math>V_4</math>, a 15kΩ resistor from input <math>V_3</math>, and a 30kΩ feedback resistor from the output <math>V_o</math>. The output of the op-amp is <math>V_o</math>.</p>
<b>5.17</b>	$\frac{v_o}{v_i} = -40$
<b>5.18</b>	$I_o = -5[\text{mA}]$ , $V_o = 5[\text{V}]$
<b>5.19</b>	$V_o = 4 V_i$
<b>5.20</b>	$v_s = -0.8[\text{V}]$
<b>5.21</b>	$V_o = -15 V_1 - 2 V_2$
<b>5.22</b>	$a = \frac{1}{3}$ , $b = \frac{1}{2}$ , $d = \frac{3}{2}$
<b>5.23</b>	$R = 5[\text{k}\Omega]$
<b>5.24</b>	$R_1 = 5[\text{k}\Omega]$ , $R_2 = 5[\text{k}\Omega]$
<b>5.25</b>	$V_o = -8 V_1 - 6 V_2$
<b>5.26</b>	$I_o = 1[\text{mA}]$

## Chapter 06

번호	답
6.1	(a) $G(s) = \frac{1}{s+3}$ (b) $F(s) = \frac{1}{s^2}$ (c) $H(s) = \frac{s}{s^2+25}$
6.2	(a) $G(s) = 3$ (b) $F(s) = \frac{2}{s^2}e^{-3s}$ (c) $H(s) = \frac{1}{s+3}e^{-2(s+3)}$ (d) $H(s) = \frac{e^{-2s}}{s^2+1}$
6.3	(a) $F(s) = \frac{2}{(s+3)^2+4}$ (b) $G(s) = e^{-2(s+2)}\left\{\frac{1}{(s+2)^2} + \frac{1}{s+2}\right\}$ (c) $H(s) = \frac{1}{(s+3)^2}$
6.4	(a) $F(s) = \frac{s+2}{(s+2)^2+4} + \frac{1}{(s+3)^3}$ (b) $F(s) = \frac{s^2+8s+115}{(s^2+6s+109)^2}$ (c) $G(s) = \frac{1}{(s+4)^2} + \frac{(s+4)e^{-s}}{(s+3)^2}$ (d) $F(s) = e^{-3} \cdot \frac{2e^{-s}}{(s+3)^2+4}$
6.5	(a) $G(s) = \frac{s+3}{(s+3)^2+10^2}$ (b) $F(s) = 3 + \frac{2s}{(s+5)^3}$ (c) $F(s) = \frac{s+2}{(s+2)^2+2^2} + \frac{1}{(s+3)^2}$ (d) $F(s) = \frac{1}{s(1+e^{-s})}$
6.6	(a) $G(s) = \frac{1}{s(1+e^{-s})}$ (b) $F(s) = \frac{1-e^{-s}}{(1+e^{-s})s^2}$

<b>6.7</b>	<p>(a) <math>F(s) = \frac{1 - e^{-s} + e^{-2s} - e^{-3s}}{s}</math></p> <p>(b) <math>F(s) = \frac{1 - e^{-s} - e^{-3s} + e^{-4s}}{s^2}</math></p>
<b>6.8</b>	<p>(a) <math>f(0) = 1, f(\infty) = 4</math></p> <p>(b) <math>f(0) = 0, f(\infty) = 0</math></p> <p>(c) <math>f(0) = 0, f(\infty) = 4</math></p>
<b>6.9</b>	<p>(a) <math>f(t) = (3 - 5e^{-t} + 2e^{-2t})u(t)</math></p> <p>(b) <math>f(t) = (1 - e^{-(t-2)})u(t-2)</math></p> <p>(c) <math>f(t) = \left(2 - \frac{7}{3}e^{-t} + \frac{1}{3}e^{-4t}\right)u(t)</math></p> <p>(d) <math>f(t) = \{3 - 4e^{-t} + e^{-3t}\}u(t) - \{3 - 4e^{-(t-3)} + e^{-3(t-3)}\}u(t-3)</math></p>
<b>6.10</b>	<p>(a) <math>f(t) = \{4 - (4 - 3t)e^{-t}\}u(t)</math></p> <p>(b) <math>f(t) = (1 - t)e^{-t} \cdot u(t)</math></p> <p>(c) <math>f(t) = \{11e^{-t} - (8 + 20t)e^{-2t}\}u(t)</math></p> <p>(d) <math>f(t) = \{e^{-2t} + (1 - 5t)e^{-3t}\}u(t)</math></p>
<b>6.11</b>	<p>(a) <math>f(t) = \left(\frac{1}{2!}t^2 + \frac{1}{3!}t^3\right)e^{-t} \cdot u(t)</math></p> <p>(b) <math>f(t) = \{-3(8 - 3t)e^{-t} + 6(4 + 3t)e^{-2t}\}u(t)</math></p> <p>(c) <math>f(t) = \left\{\frac{5}{8}e^{-t} - \frac{41}{8}e^{-5t} + \frac{1}{2}(9 - 17t)e^{-3t}\right\}u(t)</math></p> <p>(d) <math>f(t) = \left\{\frac{1}{27} + \left(\frac{1}{27} + \frac{8}{9}t - \frac{2}{3}t^2\right)e^{-3t}\right\}u(t)</math></p>
<b>6.12</b>	<p>(a) <math>f(t) = \{2e^{-t} - 2(\cos 2t + \sin 2t)e^{-2t}\}u(t)</math></p> <p>(b) <math>f(t) = \{2 - 3e^{-t} + (\cos 3t + \sin 3t)e^{-2t}\}u(t)</math></p> <p>(c) <math>f(t) = \frac{1}{2}\{e^{-t}(3\sin t - \cos t) + e^{-2t}(\cos 2t - \sin 2t)\} \cdot u(t)</math></p> <p>(d) <math>f(t) = \{3(-2 + t)e^{-t} + 6(\cos 2t + \sin 2t)e^{-2t}\}u(t)</math></p>
<b>6.13</b>	<p>(a) <math>i(t) = 2e^{-5t} \cdot u(t)</math></p> <p>(b) <math>i(t) = \frac{1}{10}(1 - e^{-10t}) \cdot u(t)</math></p> <p>(c) <math>i(t) = \frac{2}{5}(1 + 4e^{-5t}) \cdot u(t)</math></p> <p>(d) <math>i(t) = \frac{1}{16}(-1 + 4t + 81e^{-4t}) \cdot u(t)</math></p>
<b>6.14</b>	<p>(a) <math>v(t) = 3(-1 + 4t + e^{-4t})u(t)</math></p> <p>(b) <math>v(t) = \frac{1}{5}\left\{e^{-2t} - \cos 4t + \frac{1}{2}\sin 4t\right\}u(t)</math></p> <p>(c) <math>v(t) = \frac{5}{4}\{-e^{-4t} + (\cos 2t + \sin 2t)e^{-2t}\} \cdot u(t)</math></p>

<b>6.15</b>	<p>(a) <math>v(t) = \frac{2}{3}(5e^{-t} - 2e^{-4t}) \cdot u(t)</math></p> <p>(b) <math>i(t) = (1 + 3t)e^{-2t} \cdot u(t)</math></p> <p>(c) <math>i(t) = 2(\cos 2t + \sin 2t)e^{-t} \cdot u(t)</math></p> <p>(d) <math>v(t) = 5(1 - 3t)e^{-3t} \cdot u(t)</math></p>
<b>6.16</b>	<p>(a) <math>v(t) = (-15 + 12t + 16e^{-t} - e^{-4t})u(t)</math></p> <p>(b) <math>v(t) = 2\{1 - (1 + 2t)e^{-2t}\}u(t)</math></p> <p>(c) <math>i(t) = \{e^{-3t} - (\cos t - 2\sin t)e^{-t}\}u(t)</math></p> <p>(d) <math>v(t) = \frac{1}{5}(3\sin 3t + 2\sin 2t)u(t)</math></p>
<b>6.17</b>	<p>(a) <math>i(t) = \frac{1}{4}\{(-3 + 2t)e^{-t} + 12e^{-2t} - 5e^{-3t}\}u(t)</math></p> <p>(b) <math>v(t) = \frac{1}{25}\{(28 - 5t)e^{-t} - 3\cos 2t + 4\sin 2t\}u(t)</math></p> <p>(c) <math>i(t) = (\cos t + 8\sin t)e^{-2t}</math></p> <p>(d) <math>i(t) = \{3 - (2\cos t + \sin t)e^{-t}\}u(t)</math></p>



## Chapter 07




번호	답
7.1	i) $0 \leq t \leq 2\mu s$ $v(t) = 2.5 \times 10^8 t^2$ ii) $2\mu s \leq t \leq 6\mu s$ $v(t) = 1.5 \times 10^3 t - 1.25 \times 10^8 t^2 - 1.5 \times 10^{-3} [V]$ iii) $t \geq 6\mu s$ $v(t) = 3 [mV]$
7.2	(a) i) $t \leq 0$ $v(t) = 10 [V]$ ii) $0 \leq t \leq 5ms$ $v(t) = 2 \times 10^3 t + 10 [V]$ iii) $t \geq 5ms$ $v(t) = 20 [V]$ (b) $p_s(t) = 0$
7.3	(a) i) $0 \leq t \leq 3\mu s$ $v(t) = \frac{50}{3} [V]$ ii) $3\mu s \leq t \leq 6\mu s$ $v(t) = -\frac{50}{3} [V]$ (b) <p style="text-align: center;">(b)</p>
7.4	i) $t \leq 0$ $i(t) = 0$ ii) $0 \leq t \leq 3ms$ $i(t) = \frac{10^6}{6} t^2$ iii) $3ms \leq t \leq 6ms$ $i(t) = 10^3 t - 1.5$ iv) $6ms \leq t \leq 9ms$ $i(t) = 3 \times 10^3 t - \frac{10^6}{6} t^2 - 18 + 6 + 4.5 = 3 \times 10^3 t - \frac{10^6}{6} t^2 - 7.5$ v) $t \geq 9ms$ $i(t) = 6 [A]$

7.5	
7.6	<p>i) <math>t \leq 0 \quad p(t) = 0</math></p> <p>ii) <math>0 &lt; t &lt; 1s \quad p(t) = \frac{1}{5}t[\text{W}]</math></p> <p>iii) <math>1s \leq t \leq 2s \quad p(t) = 0.2(t-1)[\text{W}]</math></p> <p>iv) <math>t \geq 2s \quad p(t) = 0</math></p>
7.7	$C_{eq} = \frac{18}{11}[\mu\text{F}]$
7.8	$L_{eq} = 3[\text{mH}]$
7.9	$C_{eq} = \frac{8}{9}[\mu\text{F}]$
7.10	$L_{eq} = 1.5[\text{mH}]$
7.11	$L_{eq} = 3.6[\text{mH}]$
7.12	$L_{eq} = 10[\text{mH}]$
7.13	$C_{eq} = 3.6[\mu\text{F}]$
7.14	$W_L = 8[\text{J}], \quad W_C = 400[\text{J}]$
7.15	$W_L = 32[\text{J}], \quad W_C = 256[\text{J}]$
7.16	$W_L = 98[\text{J}], \quad W_C = 25[\text{J}]$
7.17	$W = 7.7[\text{nJ}]$
7.18	$W = 252[\mu\text{J}]$
7.19	$V_{eq} = \frac{14}{3}[\text{V}]$
7.20	<p>연결후 저장된 에너지 : <math>W = \frac{1}{2} C_{eq} \times V_{eq}^2 = \frac{121}{4} \mu\text{J}</math></p> <p>연결함으로 인해 저장에너지가 <math>15/4[\mu\text{J}]</math> 감소함.</p>
7.21	$W = 2[\mu\text{J}]$
7.22	$W - W' = 57[\text{J}]$
7.23	<p><math>i_1(t) = 2.4e^{-2t} + 1.6[\text{mA}]</math></p> <p><math>i_2(t) = 3.6e^{-2t} - 1.6[\text{mA}]</math></p>


<b>7.24</b>	$v(t) = 4.8 \sin 4t [mV], \quad i(t) = 50(1 - \cos 4t) [mA]$
<b>7.25</b>	$v(t) = -20 \exp(-10^3 t) [mV], \quad i_L(t) = 5 \exp(-10^3 t) - 3 [mA]$
<b>7.26</b>	$v_1(t) = \frac{1}{3}(2e^{-2t} + 1), \quad v_2(t) = \frac{4}{3}(e^{-2t} + 2)$
<b>7.27</b>	$v_x(t) = \sin 10^3 t [V], \quad i_o(t) = 0.25(1 - \cos 10^3 t) [A]$
<b>7.28</b>	$i_x = -16e^{-2t} [\mu A]$
<b>7.29</b>	$v_c(t) = \frac{2}{9} \{ 10 \exp(-10^3 t) - 1 \}, \quad i_s(t) = -\frac{80}{3} \exp(-10^3 t) [mA]$
<b>7.30</b>	$v_x = 4 \cos(10^3 t) [mV]$
<b>7.31</b>	
<b>7.32</b>	
<b>7.33</b>	

## Chapter 08

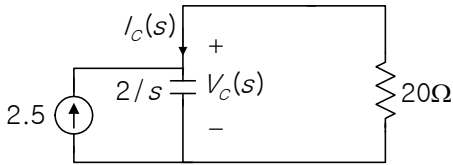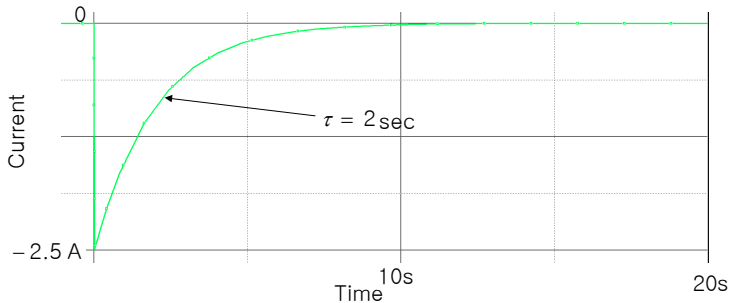번호	답
8.1	<p>(a) <math>v_C(t) + 30 \frac{d}{dt} v_C(t) = 0</math></p> <p>(b) <math>i(t) = 0.2e^{-t/30} [\text{A}]</math></p> <p>(c) <math>p_R(t) = 2e^{-t/15}</math></p> <p>(d) <math>W_R = 30 [\text{J}]</math></p>
8.2	<p>(a)</p>  <p>(b) <math>i_C(t) = -0.25e^{-0.1t}</math></p> <p>(c) <math>v_C(t) = 5e^{-0.1t}</math></p> <p>(d) <math>W_R = 6.25 [\text{W}]</math></p>
8.3	<p>(a) <math>W_C = 25 [\text{J}]</math></p> <p>(b) <math>v_C(t) + 4i_C(t) = 0</math></p> <p>(c) <math>i_C(t) = -5e^{-2t} [\text{A}]</math></p> <p>(d) <math>W_R = 25 [\text{J}]</math></p>
8.4	<p>(a) <math>i_C(t) = -2.5e^{-t/2} \cdot u(t) [\text{A}]</math></p> <p>(b)</p> 
8.5	<p>(a) <math>v_C(t) = 4 [\text{V}], i_C(t) = 0</math></p> <p>(b) <math>v_C(t) = 4e^{-0.4t} [\text{V}], i_C(t) = -0.8e^{-0.4t} [\text{A}]</math></p>

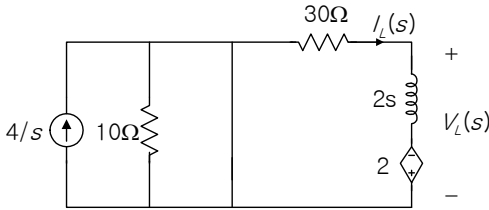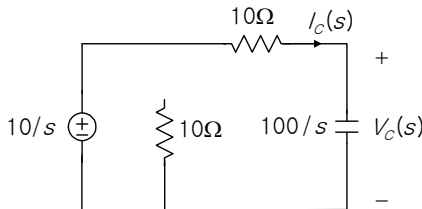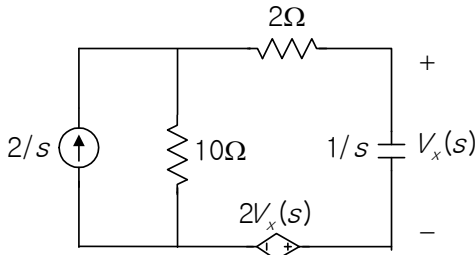
<b>8.6</b>	$t < 0 : i_x(t) = 0, t > 0 : i_x(t) = -0.8e^{-10t} \text{ [A]}$
<b>8.7</b>	<p>(a) <math>i_L(t) = 2 \text{ [A]}</math></p> <p>(b) <math>\frac{d}{dt}i_L(t) + 100i_L(t) = 0</math></p> <p>(c) <math>i_L(t) = 2e^{-100t} \text{ [A]}</math></p>
<b>8.8</b>	<p>(a) <math>i_L(t) = 1 \text{ [A]}, v_L(t) = 0</math></p> <p>(b)</p>  <p>(c) <math>i_L(t) = e^{-15t} \text{ [A]}, v_L(t) = -30e^{-15t} \text{ [V]}</math></p> <p>(d) <math>W_R = 1 \text{ [J]}</math></p>
<b>8.9</b>	<p>(a) <math>W_L = 0.45 \text{ [J]}</math></p> <p>(b) <math>i_L(t) = 3e^{-100t} \text{ [A]}, v_L(t) = -30e^{-100t} \text{ [V]}</math></p> <p>(c) <math>W_L = \frac{9}{20} \text{ [J]}</math></p>
<b>8.10</b>	<p>(a) <math>i_L(t) = 2e^{-10t} \text{ [A]}</math></p> <p>(b) <math>i_L(t) = 2e^{-10t} \cdot u(t) \text{ [A]}</math></p>
<b>8.11</b>	<p>(a) <math>v_C(t) = i_C(t) = 0</math></p> <p>(b)</p>  <p>(c) <math>i_C(t) = e^{-10t}, v_C(t) = 10(1 - e^{-10t})</math></p> <p>(d) <math>W_C = 0.5 \text{ [J]}</math></p>
<b>8.12</b>	<p>(a)</p> 

	(b) $v_x(t) = 4(1 - e^{-t/4}) \cdot u(t)$
<b>8.13</b>	(a) $i_C(t) = 2e^{-10t} [\text{A}]$ (b) $i_C(t) = 2e^{-10t} [\text{A}]$
<b>8.14</b>	$v_x(t) = \frac{8}{5}e^{-t/5} \cdot u(t) [\text{V}]$
<b>8.15</b>	$v_x(t) = 5 - 2.5e^{-t/2} [\text{V}]$
<b>8.16</b>	$t < 0 : i_C(t) = 0, t > 0 : i_C(t) = 0.3e^{-0.1t} [\text{A}]$
<b>8.17</b>	$t < 0 : v_L(t) = 0, i_L(t) = 0$ $t > 0 : i_L(t) = 2(1 - e^{-45t}) [\text{A}], v_L(t) = 180e^{-45t} [\text{V}]$
<b>8.18</b>	$t < 0 : i_L(t) = 0, v_L(t) = 0$ $t > 0 : v_L(t) = \frac{20}{3}e^{-10t} [\text{V}], i_L(t) = \frac{10}{3}(1 - e^{-t}) [\text{A}]$
<b>8.19</b>	<p>(a) <math>i_L(0_-) = 0, v_R(0_+) = 0</math> (b) <math>v_R(t) = 5(1 - 10^{-10^4 t}) [\text{V}]</math></p> <p>(c) </p> <p>(d) <math>v_R(t) = 5(1 - e^{-10^4 t}) [\text{V}]</math></p>
<b>8.20</b>	$t \leq 0 : v_o = 0$ $0 < t \leq 10^{-4} : v_o(t) = 10(1 - e^{-10^4 t}) [\text{V}]$ $t > 10^{-4} : v_o(t) = 10 - 10e^{-10^4 t} - 10 + 10e^{-10^4(t - 10^{-4})} = 10(e - 1) \cdot e^{-10^4 t}$
<b>8.21</b>	<p>(a) <math>v_C(t) = 10 [\text{V}]</math> (b) <math>10i_C + v_C = 20</math> (c) <math>10\frac{d}{dt}i_C(t) + 5i_C(t) = 0</math> (d) <math>i_C(t) = e^{-0.5t} [\text{A}]</math> (e) <math>v_C(t) = 10 - 10e^{-0.5t} [\text{V}]</math></p>
<b>8.22</b>	<p>(a) <math>v_x(t) = 5 - 2.5e^{-t/2} [\text{V}]</math> (b) <math>v_x(t) = 5 - 2.5e^{-0.5t} [\text{V}]</math></p>
<b>8.23</b>	$v_L(t) = -30e^{-20t} [\text{V}]$
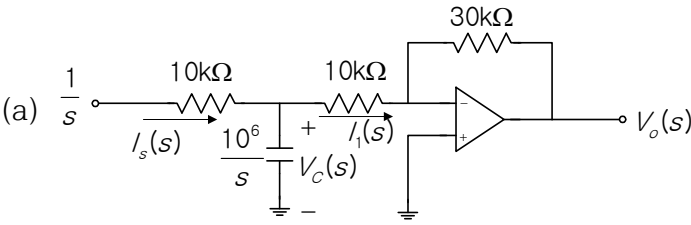
<b>8.24</b>	$v_L(t) = 10e^{-t} \text{ [V]}$
<b>8.25</b>	$i_L(t) = 2 - e^{-1200t} \text{ [A]}$
<b>8.26</b>	$v_L(t) = -20e^{-20t} \cdot u(t) \text{ [V]}$
<b>8.27</b>	(a) $i_L(t) = 2 - e^{-250t} \text{ [A]}$ (b) $W_L = 72 \text{ [mJ]}$
<b>8.28</b>	$v_o(t) = 2(1 - e^{-2000t}) \cdot u(t) \text{ [V]}$
<b>8.29</b>	 <p>(a) <math>\frac{1}{s}</math> <math>10\text{k}\Omega</math> <math>I_s(s)</math> <math>10^6/s</math> <math>V_C(s)</math> <math>10\text{k}\Omega</math> <math>I_i(s)</math> <math>30\text{k}\Omega</math> <math>V_o(s)</math></p> <p>(b) <math>v_o(t) = -1.5(1 - e^{-200t}) \text{ [V]}</math></p> <p>(c) <math>\frac{d}{dt}v_C(t) + 200v_C(t) = 100</math></p> <p>(d) <math>\frac{d}{dt}v_o(t) + 200v_o(t) = -300</math></p> <p>(e) <math>v_C(t) = 0.5(1 - e^{-200t}) \text{ [V]}</math>, <math>v_o(t) = -1.5(1 - e^{-200t}) \text{ [V]}</math></p>
<b>8.30</b>	$t < 0 : v_o(t) = 0$ , $0 \leq t < 1\text{ms} : v_o(t) = 10^3t + 1 \text{ [V]}$ $1\text{ms} \leq t < 2\text{ms} : v_o(t) = -10^3t + 1 \text{ [V]}$ , $t \geq 2\text{ms} : v_o(t) = 0$
<b>8.31</b>	$v_o(t) = (3 - e^{-20t})u(t) - \{3 - e^{-20(t-0.2)}\}u(t-0.2)$
<b>8.32</b>	$v_o(t) = -4\cos(10^3t)u(t)$

## Chapter 09






번호	답
9.1	(a) $f(t) = e^{-2t} \cdot \sin 2t$ (b) $h(t) = 5(1 + 2t) \cdot e^{-2t}$ (c) $g(t) = 2 + e^{-2t} - 3e^{-4t}$
9.2	(a) $i(t) = 0, v(t) = 2V$ (b) $\frac{d^2}{dt^2}v(t) + 2\frac{d}{dt}v(t) + v(t) = 0$ (c) 임계제동으로 동작함 (d) $v(t) = 2(1 + t)e^{-t}, i(t) = 2te^{-t}$
9.3	(a) $i(t) = -50(e^{-20t} - e^{-100t}) \text{ [mA]}$ (b) $v(t) = \frac{5}{4}(5e^{-20t} - e^{-100t})$
9.4	(a) $i(t) = 0, v(t) = 10$ (b) $i(t) = 10e^{-t} \cdot \sin t \text{ [A]}$ (c) $v(t) = 10e^{-t}(\cos t + \sin t)$
9.5	(a) $i(t) = 0, v(t) = 10$ (b) $i(t) = 5e^{-2t} \cdot \sin 2t \text{ [A]}$ (c) $v(t) = 10e^{-2t} \cdot \cos 2t \text{ [V]}$
9.6	(a) $v_R(t) = 2e^{-10^3 t} \sin 10^4 t \cdot u(t) \text{ [V]}$ (b) $v_R(t) _{max} = 2e^{-0.05\pi}$
9.7	$i_L(t) = 3.2t \cdot e^{-20t} \text{ [A]}$
9.8	(a) $i(t) = 0, v(t) = 0$ (b) $v(t) = 10(1 - 2e^{-2t} + e^{-4t}) \text{ [V]}$
9.9	$v(t) = 10[1 - e^{-7.125t}(\cos 7.02t + 1.02 \sin 7.02t)]$
9.10	(a) $i_L(t) = 0, v_C(t) = 0$ (b) $\frac{d^2}{dt^2}v_C(t) + 2\frac{d}{dt}v_C(t) + v_C(t) = 20$ (c) $v_C(t) = 10 - 10(1 + t)e^{-t}$
9.11	(a) $i(t) = 2.5\{1 - e^{-t}(\cos t + \sin t)\} \cdot u(t) \text{ [A]}$ (b) $i(t) _{max} = 2.5(1 + e^{-\pi})$

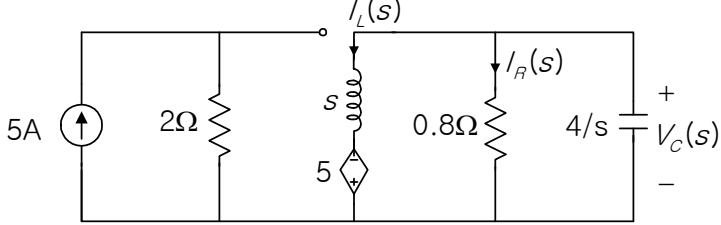9.12	$i(t) = \frac{1}{2\sqrt{3}} \{ e^{-(4-2\sqrt{3}) \times 10^4 t} - e^{-(4+2\sqrt{3}) \times 10^4 t} \}$
9.13	(a) $i_L = 0, v_C(t) = 10[\text{V}]$ (b) $i_L(t) = 5te^{-t} [\text{A}]$
9.14	$v_C(t) = 5 + 15e^{-2t} - 5e^{-3t} [\text{V}], i_L(t) = 2.5(1 - 3e^{-2t} + 2e^{-3t}) [\text{A}]$
9.15	(a) $i_L(t) = -1.4e^{-5t} \left( \frac{1}{\sqrt{13}} \sin 5\sqrt{13}t \right) [\text{A}]$ (b) $R_L = \frac{100}{3} [\Omega]$
9.16	(a) $v(t) = 6 - 8e^{-t} + 2e^{-4t}$ (b) $v(t) = 12 + \{ (18e^4 + 24e^3 - 6) + (8 - 32e^3 - 24e^4)t \} e^{-4t}$
9.17	(a) $i_L(t) = 5, v_C(t) = 0$ (b)  (c) $i_R(t) = -\frac{25}{3}(e^{-t} - e^{-4t}) \cdot u(t) [\text{A}]$
9.18	(a) $v_C(t) = -20e^{-t} \cdot \sin t \cdot u(t) [\text{V}]$ (b) $p_R(t) = 100e^{-2t}(1 - \cos 2t)$ (c) $W_R = 25[\text{J}]$
9.19	(a) $i_L(t) = 5, v_C(t) = 0$ (b) $i_L(t) = 5(\sqrt{2} + 1)e^{-(2-\sqrt{2})t} + 5(1 - \sqrt{2})e^{-(2+\sqrt{2})t}$
9.20	(a) $i_L(t) = 0, v_C(t) = 0$ (b) $v_C(t) = \frac{20}{3}(e^{-t} - e^{-4t})u(t) [\text{V}], i_L(t) = \left( 5 - \frac{20}{3}e^{-t} + \frac{5}{3}e^{-4t} \right) \cdot u(t) [\text{A}]$
9.21	$i_L(t) = 5\{1 + (1+t)e^{-t}\} \cdot u(t) [\text{A}]$
9.22	(a) $i_L(t) = 0, v_C(t) = 0$ (b) $\frac{d^2}{dt^2}i_L(t) + 4\frac{d}{dt}i_L(t) + 8i_L(t) = 40$ (c) 부족제동으로 동작함 (d) $v_C(t) = 20e^{-2t}\sin 2t[\text{V}]$

<b>9.23</b>	<p>(a) <math>i_L(t) = -5</math>, <math>v_C(t) = 0</math></p> <p>(b) <math>i_L(t) = 5 - \frac{10}{3}(4e^{-t} - e^{-4t})</math></p>
<b>9.24</b>	<p>(a) <math>v_C(0^+) = 0</math>, <math>i_L(0^+) = 0.1</math> [A], <math>i_R(0^+) = 0.16</math> [A]</p> <p>(b) <math>\left. \frac{d}{dt} v_C(t) \right _{t=0^+} = 6 \times 10^4</math>, <math>\left. \frac{d}{dt} i_L(t) \right _{t=0^+} = 0</math>, <math>\left. \frac{d}{dt} i_R(t) \right _{t=0^+} = 1.2 \times 10^3</math></p> <p>(c) <math>\frac{d^2}{dt^2} i_R(t) + 2 \times 10^3 \frac{d}{dt} i_R(t) + 10^7 i_R(t) = 1.6 \times 10^6</math></p> <p>(d) <math>i_R(t) = 0.16 + e^{-10^3 t} \{1.44 \cos(3 \times 10^3 t) + 0.88 \sin(3 \times 10^3 t)\}</math></p>
<b>9.25</b>	<p>(a) <math>i_L(t) = 5 + (2 + 4t)e^{-2t}</math> [A]</p> <p>(b) <math>v_C(t) = -24t \cdot e^{-2t}</math> [V]</p>
<b>9.26</b>	$v_1(t) = \frac{15}{2} - \frac{20}{3}e^{-t} - \frac{5}{6}e^{-4t}$ [V], $v_2(t) = 5 - \frac{20}{3}e^{-t} + \frac{5}{3}e^{-4t}$ [V]
<b>9.27</b>	<p>(a) <math>i_{L2}(0_+) = 0</math>, <math>\left. \frac{d}{dt} i_{L2}(t) \right _{t=0_+} = 10</math></p> <p>(b) <math>\frac{d^2}{dt^2} i_{L2}(t) + 6 \frac{d}{dt} i_{L2}(t) + 4 i_{L2}(t) = 0</math></p> <p>(c) <math>i_{L2}(t) = \sqrt{5} \cdot \{e^{(-3 + \sqrt{5})t} - e^{-(3 + \sqrt{5})t}\}</math></p>
<b>9.28</b>	$v_o(t) = -2e^{-100t} \cdot \sin 100t$ [V]
<b>9.29</b>	<p>(a) <math>\frac{d^2}{dt^2} v_1 + 2 \frac{d}{dt} v_1(t) + v_1(t) = 5</math></p> <p>(b) <math>v_o(t) = 5t \cdot e^{-t}</math> [V]</p>
<b>9.30</b>	<p>(a) <math>\frac{d^2}{dt^2} v_o(t) + \frac{100}{9} \frac{d}{dt} v_o(t) + \frac{100}{9} v_o(t) = v_i(t)</math></p> <p>(b) <math>v_o(0^+) = 0</math>, <math>\left. \frac{d}{dt} v_o(t) \right _{t=0^+} = 0</math></p> <p>(c) <math>v_o(t) = 5 - \frac{45}{8}e^{-10t} + \frac{5}{8}e^{-90t}</math> [V]</p>


## Chapter 10







번호	답
10.1	(a) 진폭 : $V_m = 5$ 위상 : $\theta = -83.13^\circ$ 주파수 : $\omega = 10\text{rad/s}$ (b) 진폭 : $V_m = 14.5$ 위상 : $\theta = 70^\circ$ 주파수 : $\omega = 1\text{krad/s}$ (c) 진폭 : $V_m = \sqrt{5}$ 위상 : $\theta = 165^\circ$ 주파수 : $\omega = 100\text{rad/s}$
10.2	(a) $v_1(t)$ 가 $v_2(t)$ 보다 $30^\circ$ 빠르다. (b) $v_1(t)$ 가 $v_2(t)$ 보다 $120^\circ$ 빠르다. (c) $i_1(t)$ 가 $i_2(t)$ 보다 위상이 $30^\circ$ 빠르다.
10.3	(a) $v(t) = 10\sqrt{2}\cos(t+45^\circ)$ , $i(t) = 5\sqrt{2}\cos(t-45^\circ)$ (b) $v(t) = 25\sqrt{2}\cos(4t-45^\circ)$ , $i(t) = \frac{5\sqrt{5}}{4}\cos(4t-63.4^\circ)$
10.4	(a) $\mathbf{V} = 2\sqrt{2} + j2\sqrt{2}$ (b) $\mathbf{V} = -20 + j20\sqrt{3}$ (c) $\mathbf{I} = 5 - j2\sqrt{3}$ (d) $\mathbf{I} = j\sqrt{2}$ (e) $\mathbf{I} = 5(1 + \sqrt{3}) - j5(1 + \sqrt{3})$ (f) $\mathbf{V} = \left(5 - \frac{\sqrt{3}}{20}\right) + j\left(5\sqrt{3} - \frac{1}{20}\right)$ (g) $\mathbf{I} = \sqrt{3} + j3$
10.5	(a) $v(t) = 40\cos(10t - 30^\circ)$ (b) $v(t) = 19.9\cos(10t + 15.98^\circ)$ (c) $i(t) = \cos(20t - 45^\circ)$ (d) $i(t) = 5\cos(20t + 53.13^\circ)$ (e) $v(t) = 19.32\cos(4t + 15^\circ)$ (f) $v(t) = 1.17\cos(100t + 5.9^\circ)$
10.6	(a) $v(t) = 0.329\cos(10t - 80.5^\circ)$ (b) $v(t) = 9.58\sin(10t - 43.3^\circ)$ (c) $v(t) = 0.60\cos(10t - 87.7^\circ)$ (d) $v(t) = 0.8\cos(2t - 98.13^\circ)$ (e) $v(t) = 0.745\cos(5t - 6.56^\circ)$
10.7	(a) $\frac{d^2}{dt^2}v_o(t) + 20\frac{d}{dt}v_o(t) + \frac{500}{3}v_o(t) = 10\frac{d}{dt}v_s(t)$ (b) $v_o(t) = 0.47\cos(10t + 18.4^\circ)$
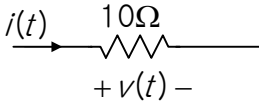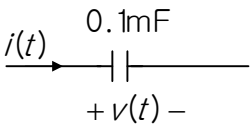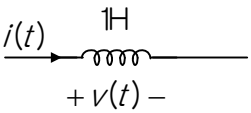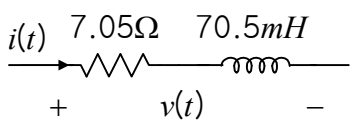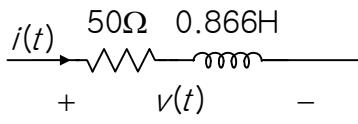
<b>10.8</b>	<p>(a) <math>\frac{d^2}{dt^2}i_L(t) + 2 \times 10^3 \frac{d}{dt}i_L(t) + 3 \times 10^6 i_L(t) = 5 \times 10^6 \cos 10^3 t</math></p> <p>(b) <math>i_L(t) = 1.77(\cos 10^3 t - 45^\circ)</math></p>
<b>10.9</b>	$I_o = 4.60 - j0.827$
<b>10.10</b>	$v_o(t) = 5 \cos(2t + 90^\circ)$ , $i(t) = 2.5 \cos 2t$
<b>10.11</b>	$v_o(t) = 1.25 \cos(10t + 38.7^\circ)$
<b>10.12</b>	$v_o(t) = 3.92 \cos(100t + 124^\circ)$
<b>10.13</b>	$v(t) = 5 \cos(10^3 t)$
<b>10.14</b>	$I_o = -j10 = 10 \angle -90^\circ$
<b>10.15</b>	$i(t) = \sqrt{2} \cos(10t - 45^\circ)$ , $v_o(t) = \sqrt{2} \cos(10t + 45^\circ)$
<b>10.16</b>	<p>(a) </p> <p>(b) </p> <p>(c) </p> <p>(d) </p> <p>(e) </p>
<b>10.17</b>	<p>(a) <math>Z_{in} = 0.5 + j0.5</math></p> <p>(b) <math>Z_{in} = 4 - j2</math></p>
<b>10.18</b>	$Z_{in} = 150 - j80$
<b>10.19</b>	<p>(a) <math>Z_{in} = 6 - j8 [\Omega]</math></p> <p>(b) <math>Z_{in} = 15 - j5 [\Omega]</math></p>

<b>10.20</b>	(a) $i_s(t) = 0.284\cos(10t - 71.6^\circ)[\text{A}]$ (b) $I_s = 2.5$
<b>10.21</b>	$v_o(t) = 2.5\cos(100t + 90^\circ)$
<b>10.22</b>	$i_o(t) = \sqrt{2}\cos(2t + 45^\circ)$
<b>10.23</b>	$I_s = 8 - j4$
<b>10.24</b>	$V_s = 4 + j4$
<b>10.25</b>	$Z = 4 + j4[\Omega]$



# Chapter 11



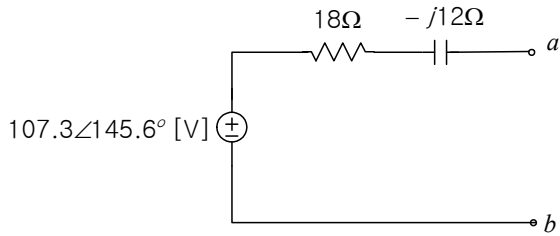
번호	답
11.1	$v_o(t) = 15.8\cos(10t + 26.6)$
11.2	$v_o(t) = 20.1\cos(t - 1.2^\circ)$
11.3	$v_o(t) = 2.74\cos(t - 8.34^\circ)$
11.4	$I_o = -0.90 + j1.07$
11.5	$I = 5.74 + j5.44$
11.6	$I = 1.42 + j0.34$
11.7	$V_o = -44 - j12 \text{ [V]}$
11.8	$V_o = 6(1 + j) \text{ [V]}$
11.9	$v_o(t) = 2.2\cos(4t - 174^\circ) \text{ [V]}$
11.10	$I_o = 3.05 \angle -165.9^\circ \text{ [A]}$
11.11	$I_o = 7.6 \angle -59.2^\circ \text{ [A]}$
11.12	$V_o = 3.58 \angle 80^\circ = 0.62 + j3.5$
11.13	$I_o = 4.5 \angle 138^\circ$
11.14	$i_x(t) = 4.01\cos(2t - 38.9^\circ)$
11.15	$v_o(t) = 6.49 \cdot \cos(4t - 36.3^\circ) \text{ [V]}$
11.16	$i_o = 4 + 0.49\cos(2t - 50.9^\circ) + 0.49\cos(4t - 119^\circ)$
11.17	$i_o \equiv 50 + 120 \cdot \cos(2 \times 10^3 t + 122^\circ) \text{ [mA]}$
11.18	$v_o(t) = 3.61\cos(10^5 t - 40.6^\circ)$
11.19	$V_o = \frac{30}{17} - j\frac{50}{17}$
11.20	 <p>The circuit diagram shows a voltage source of <math>107.3 \angle 145.6^\circ \text{ [V]}</math> in series with a <math>18\Omega</math> resistor and a <math>-j12\Omega</math> reactance. The output terminals are labeled <math>a</math> and <math>b</math>.</p>

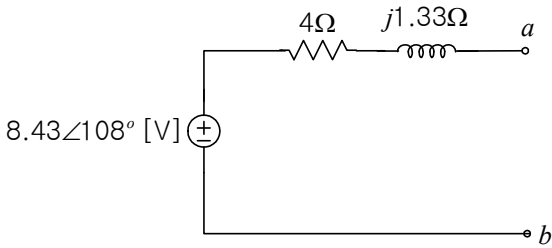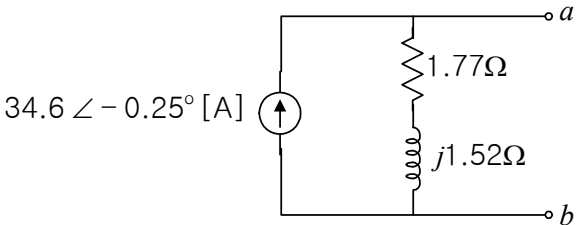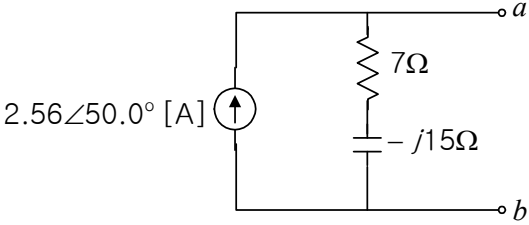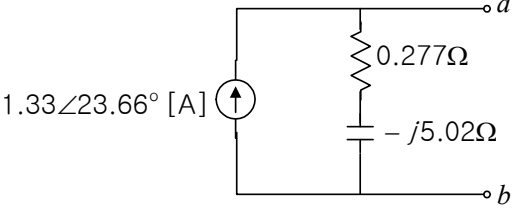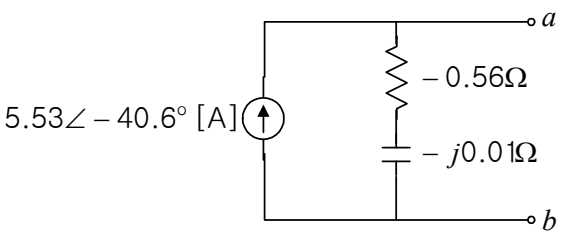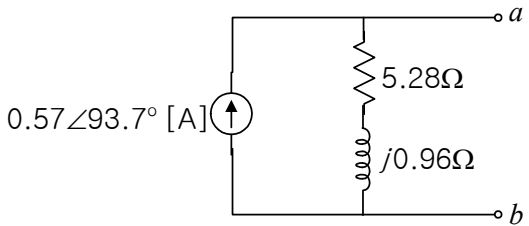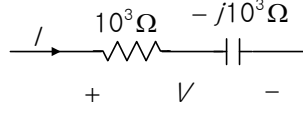11.21	
11.22	$V = (10 + j5) \cdot I + 5.59 \angle 18.4^\circ$
11.23	
11.24	
11.25	
11.26	
11.27	

<b>11.28</b>	$v_o(t) = 1.79\cos(10^3t - 153^\circ)$
<b>11.29</b>	$v_o(t) = 1.41\cos(10^3t - 129^\circ) + 71.1\cos(100t + 50.7^\circ)$
<b>11.30</b>	$\mathbf{Z}_{in} = 15(1 - j) \times 10^3 \text{ } [\Omega]$
<b>11.31</b>	$\frac{V_o}{V_s} = \frac{R_2 + R_3}{R_3} \cdot \frac{(1 + j\omega(R_2 // R_3)C_2)}{(1 + j\omega R_1 C_1) \cdot 1 + j\omega R_2 C_2)}$





## Chapter 12

번호	답
12.1	(a) $p(t) = \frac{1}{2} V_m I_m \{ \cos \theta_i + \cos(2\omega t + \theta_i) \}$ (b) $p(t) = 50(1 + \sin 20t)$
12.2	(a) $p(t) = 4.1 \cos(4t - 109.6^\circ) [\text{W}]$ (b) $p(t) = 3.175 \cos(8t) [\text{W}]$
12.3	$P_{40\Omega} = 22.5 [\text{W}]$
12.4	$R = 6.13 [\Omega]$
12.5	$P = 51.3 [\text{W}]$
12.6	(a)  (b) $P = 25 [\text{mW}]$
12.7	$P = 0$
12.8	$P = 50 [\text{W}]$
12.9	$P_{\max} = 53.6 [\text{W}]$
12.10	$R_L = \sqrt{34} [\Omega]$
12.11	(a) $Z_L = \frac{3}{2} + j\frac{1}{6}, P_{\max} = 2.31 [\text{W}]$ (b) $Z_L = 2 - j, P_{\max} = 10 [\text{W}]$
12.12	
12.13	$R = 6.33 [\Omega]$
12.14	(a) $V_{rms} = \frac{2}{\sqrt{3}} [\text{V}]$ (b) $V_{rms} = \sqrt{7/6} [\text{V}]$
12.15	(a) $I_{rms} = 10 [\text{mA}]$ (b) $I_{rms} = 5 [\text{mA}]$
12.16	(a) $\mathcal{S} = 220 \angle -30^\circ [\text{VA}], P = 110\sqrt{3} [\text{W}], Q = -220 [\text{VAR}],$


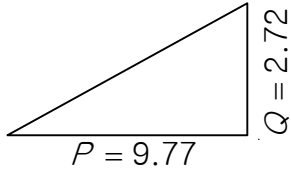
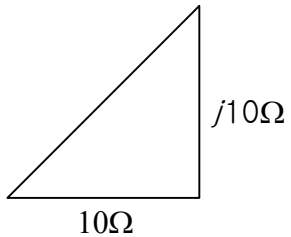
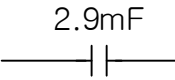
	$pf = \frac{\sqrt{3}}{2}(\text{leading, 진상})$ <p>(b) <math>\mathbf{S} = 121 \angle 60^\circ</math> [VA], <math>P = \frac{121}{2}</math> [W], <math>Q = \frac{121\sqrt{3}}{2}</math> [VAR], <math>pf = 0.5(\text{lagging, 지상})</math></p> <p>(c) <math>\mathbf{S} = 800 \angle 60^\circ</math> [VA], <math>P = 400</math> [W], <math>Q = 400\sqrt{3}</math> [VAR], <math>pf = 0.5(\text{lagging, 지상})</math></p> <p>(d) <math>\mathbf{S} = 6.4 \times 10^3 \angle 30^\circ</math> [VA], <math>P = 3.2 \times \sqrt{3}</math> [kW], <math>Q = 3.2</math> [kVAR],</p> $pf = \frac{\sqrt{3}}{2}(\text{lagging, 지상})$ <p>(e) <math>\mathbf{S} = 45 \angle -30^\circ</math> [VA], <math>P = 22.5\sqrt{3}</math> [W], <math>Q = -22.5</math> [VAR],</p> $pf = \frac{\sqrt{3}}{2}(\text{leading, 진상})$
12.17	<p>(a) <math>\mathbf{S} = 260 + j100</math> [VA]</p> <p>(b) <math>\mathbf{S} = 300 + j100\sqrt{27}</math> [VA]</p> <p>(c) <math>\mathbf{S} = 1.21 \angle 30^\circ</math> [kVA]</p> <p>(d) <math>\mathbf{S} = \frac{4}{14} + j\frac{6}{13}</math> [kVA]</p> <p>(e) <math>\mathbf{S} = 1.6 - j1.43</math> [kVA]</p>
12.18	$\mathbf{S} = j5.52$ [kVA]
12.19	$pf = 0.16(\text{lagging, 지상})$ , $P_{\text{전원}} = 29.1$ [W]
12.20	$I_m = 53.5$ [A], $\mathbf{S} = 8.33$ [kVA]
12.21	$\mathbf{S} = 40.6 \angle -81.9^\circ$ [VA]
12.22	
12.23	$\mathbf{V}_o = 40.5 \angle -18.9^\circ$ [V <sub>rms</sub> ]
12.24	 <p>, <math>pf = \cos 45^\circ = 0.707(\text{지상})</math></p>
12.25	





<b>12.26</b>	<p>(a) <math>pf = \frac{1}{\sqrt{2}}</math>, 지상(lagging)</p> <p>(b) <math>pf_{total} = \frac{1}{\sqrt{5}}</math> (진상)</p>
<b>12.27</b>	<p>(a) <math>\mathcal{S}_{\text{전원}} = 880 + j348 \text{ [VA]}</math></p> <p>(b) <math>pf = 0.93</math>(지상)</p> <p>(c) <math>C = 194 \text{ } [\mu\text{F}]</math></p>


## Chapter 13

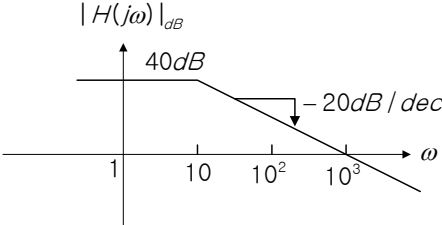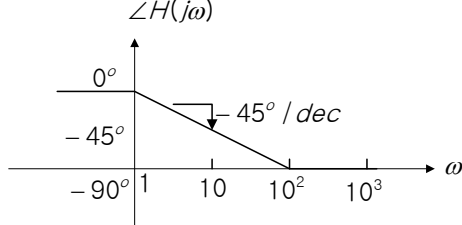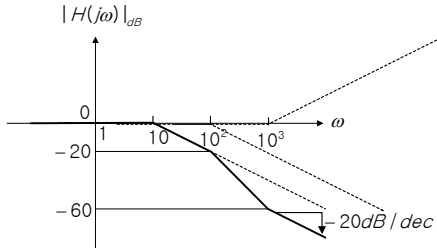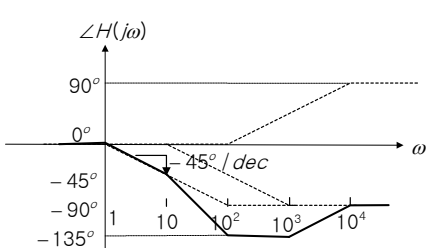번호	답
13.1	(a) $T(j\omega) = \frac{1}{1 + j\omega RC}$ (b) $T(j\omega) = \frac{j\omega L}{R + j\omega L}$
13.2	(a) $T(s) = \frac{R + sL}{2R + s(R^2C + L) + s^2RLC}$ (b) $T(s) = \frac{s^2RLC}{R + sL + s^2RLC}$
13.3	(a) $H(j\omega) = \frac{100\omega}{100\omega + j(50\omega^2 - 2)}$ (b) $H(j\omega) = \frac{8\omega^2}{(7\omega^2 + 4) - j14\omega}$
13.4	<div> <div>           (a)              [크기에 대한 보데선도]         </div> <div>             [위상에 대한 보데선도]         </div> </div> <div> <div>           (b)              [크기에 대한 보데선도]         </div> <div>             [위상에 대한 보데선도]         </div> </div>



	<div data-bbox="351 302 391 347">(c)</div> <div data-bbox="399 347 853 627"> </div> <div data-bbox="486 649 774 694">[크기에 대한 보데선도]</div> <div data-bbox="917 347 1404 627"> </div> <div data-bbox="1013 638 1316 683">[위상에 대한 보데선도]</div> <div data-bbox="351 750 391 795">(d)</div> <div data-bbox="422 784 861 1187"> </div> <div data-bbox="494 1198 790 1243">[크기에 대한 보데선도]</div> <div data-bbox="901 851 1340 1142"> </div> <div data-bbox="965 1164 1268 1209">[위상에 대한 보데선도]</div>
<div data-bbox="223 1568 295 1624">13.5</div>	<div data-bbox="351 1288 391 1332">(a)</div> <div data-bbox="399 1332 821 1646"> </div> <div data-bbox="478 1657 750 1702">크기에 대한 보데선도</div> <div data-bbox="925 1344 1404 1590"> </div> <div data-bbox="1021 1601 1308 1646">위상에 대한 보데선도</div>

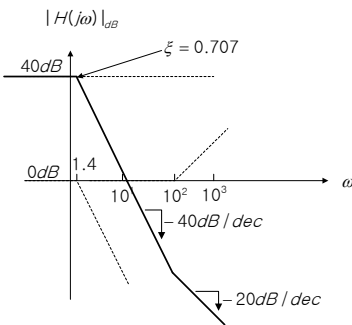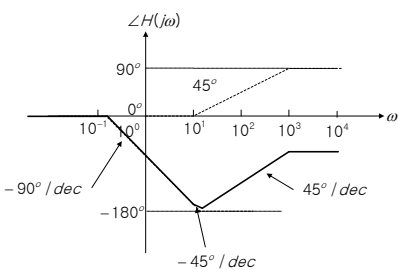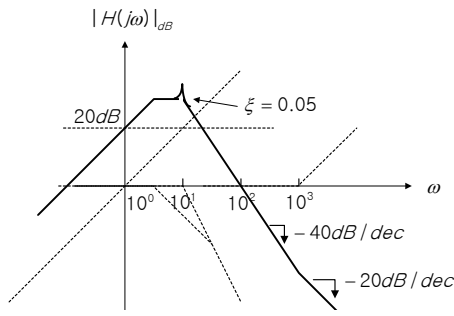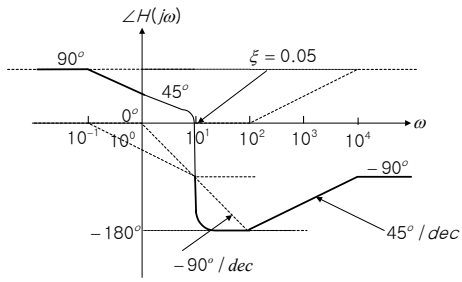	<p>(b)</p>  <p>크기에 대한 보데선도</p>  <p>위상에 대한 보데선도</p> <p>(c)</p>  <p>크기에 대한 보데선도</p>  <p>위상에 대한 보데선도</p>
13.6	<p>(a) <math>T(s) = \frac{10(1+s/10)}{(1+s/10^2)(1+s/10^3)}</math></p> <p>(b) <math>T(s) = \frac{s^2(1+s/10^4)}{(1+s/10)^2(1+s/10^2)}</math></p>
13.7	$T(s) = \frac{10^3(1+s/10)}{s(1+s/10^3)}$
13.8	$T(s) = \frac{1}{s(1+s/10^3)}$
13.9	$T(s) = \frac{1+s/10^5}{(1+s/10)(1+s/10^2)}$
13.10	$\omega_o = 5 \times 10^4 [\text{rad}], Z_{in}(j\omega_o/2) = 10^3 + j480 [\Omega], Z_{in}(j2\omega_o) = 10^3 + j1995 [\Omega]$
13.11	<p>(a) <math>T(s) = \frac{1}{(1+s/10^3)(1+s/10^6)}</math></p> <p>(b) 영점은 없음, 극점 : <math>s = -10^3, -10^6</math></p>

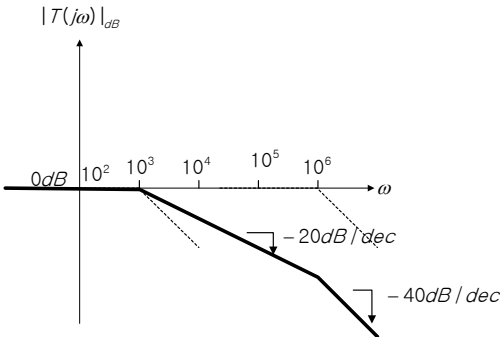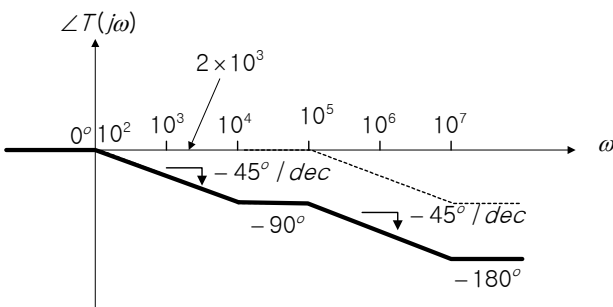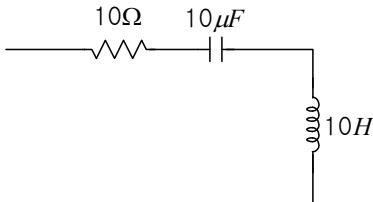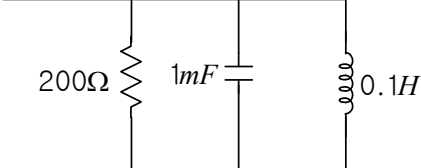	<p>(c)</p>  <p>크기에 대한 보데선도</p> <p>(d)</p>  <p>위상에 대한 보데선도</p>
13.12	
13.13	$\omega_o = 0.786 \text{ [rad/s]}$
13.14	
13.15	<p>(a) <math>\omega_o = 4.84 \times 10^3 \text{ [rad/s]}</math></p> <p>(b) <math>\omega_o = \sqrt{\frac{1}{LC} - \left(\frac{R}{L}\right)^2}</math></p>


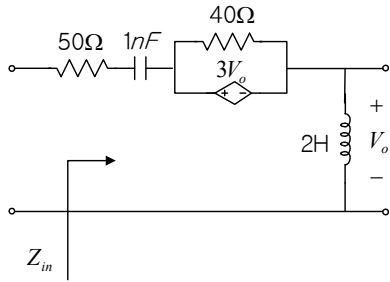
13.16	$\omega_o = \sqrt{3}[\text{rad/s}]$
13.17	$\omega_o = \sqrt{\frac{1}{LC - R_2^2 C^2}}$
13.18	(a) $\omega_o = 0.5[\text{rad/s}]$ (b) $Q = 0.5$
13.19	(a) $\omega_o = 1.58[\text{rad/s}]$ , $Q = 0.2$ , $B = 8[\text{rad/s}]$ (b) $\omega_o = 5 \times 10^3[\text{rad/s}]$ , $Q = 20$ , $B = 250[\text{rad/s}]$
13.20	(a) 고역통과필터, $\omega_c = 1000[\text{rad/s}]$ (b) 저역통과필터, $\omega_c = 1000[\text{rad/s}]$
13.21	(a) 저역통과필터, $\omega_c = 1000[\text{rad/s}]$ , (b) 고역통과필터, $\omega_c = 1000[\text{rad/s}]$
13.22	$R = 0.42[\Omega]$ , $L = 0.21 [\text{mH}]$ , $C = 40 [\mu\text{F}]$ 의 직렬회로
13.23	$\omega_o = \sqrt{2}$ , $B = 2[\text{rad/s}]$
13.24	$\omega_o = 1\text{rad/s}$ , $\omega_1 = 0.303\text{rad/s}$ , $\omega_2 = 3.30\text{rad/s}$ 인 대역통과필터
13.25	$\lim_{s \rightarrow 0} H(s) = 0$ , $\lim_{s \rightarrow \infty} H(s) = 0$ , 대역통과필터
13.26	(a) $T(s) = \left(1 + \frac{R_1}{R_2}\right) \cdot \frac{sR_i C_i}{1 + sR_i C_i}$ , 고역통과필터 (b) $T(s) = \frac{1}{1 + s(R_1 + R_2)C_2 + s^2 R_1 R_2 C_1 C_2}$ , 저역통과필터
13.27	(a) $Z_{in}(j\omega) = 5 + j(8\omega - 10^7/\omega)$ (b)  (c) $Z_{in}(j\omega) = 50 + j(8\omega - 10^9/\omega)$
13.28	(a) $T(s) = \frac{s}{1 + s}$ (b) $K_m = 10^3$ , $R = 1[\text{k}\Omega]$

# Chapter 14

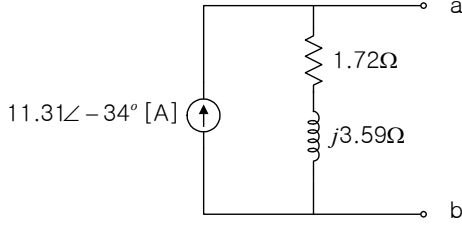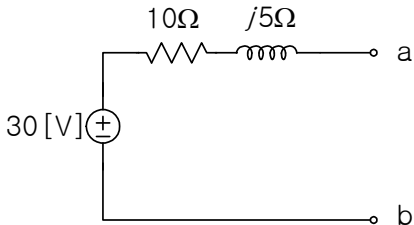번호	답
14.1	$Z_{in} = 1.94 - j0.06 [\Omega]$
14.2	(a) $L_{eq} = 36[\text{H}]$ (b) $L_{eq} = \frac{100}{13}[\text{H}]$
14.3	$V_1 = (R_1 + j\omega L_1) \cdot I_1 + j\omega M \cdot I_2$ $V_2 = j\omega M \cdot I_1 + (R_2 + j\omega L_2) \cdot I_2$
14.4	$v_o(t) = 111.5 \cos(10t - 99.5^\circ) [\text{V}]$
14.5	$v_o(t) = 3.92 \cos(2t - 71^\circ) [\text{V}]$
14.6	$V_1 = 3.98 \angle 34^\circ$ , $V_2 = 4.14 \angle -39^\circ$
14.7	
14.8	
14.9	$v_o(t) = 1.12 \sin(2t - 33.4^\circ)$
14.10	$W_t = 0.61 [\text{J}]$
14.11	$W_t = 28.3 [\mu\text{J}]$
14.12	$P_{10\Omega} = 15.14[\text{W}]$
14.13	$Z_{in} = 23.92 - j6.49$
14.14	$Z_{in} = 0.088 + j8.67 [\Omega]$
14.15	$I_1 = 74 \angle 42.0^\circ [\text{mA}]$ , $I_2 = 222 \angle 42.0^\circ [\text{mA}]$

<b>14.16</b>	$V_1 = -5.27, V_2 = -1.32[\text{V}]$
<b>14.17</b>	$V_o = 24$
<b>14.18</b>	$S = (74 - j34) \times 10^3[\text{VA}]$
<b>14.19</b>	$n = 0.485$
<b>14.20</b>	$Z_{in} = 5.7 - j1.9 [\Omega]$
<b>14.21</b>	$V_o = 2.92 \angle 15.26^\circ [\text{V}]$
<b>14.22</b>	$P_L = 44.3[\text{kW}]$
<b>14.23</b>	$I_1 = 0.83 \angle -88.7^\circ [\text{A}], I_2 = 0.454 \angle -157^\circ [\text{A}]$
<b>14.24</b>	$Z_{eq} = 2 + j$
<b>14.25</b>	$P_{2\Omega} = 367[\text{W}], P_{5\Omega} = 1.81[\text{W}], P_{10\Omega} = 14.5[\text{W}]$
<b>14.26</b>	$I_1 = 0.017 \angle -11.63^\circ [\text{A}], I_2 = 0.083 \angle -11.63, P_L = 0.069[\text{W}]$
<b>14.27</b>	$Z_{in} = 1.6 + j1.6 [\Omega]$
<b>14.28</b>	$P_L = 9.59[\text{W}]$

# Chapter 15

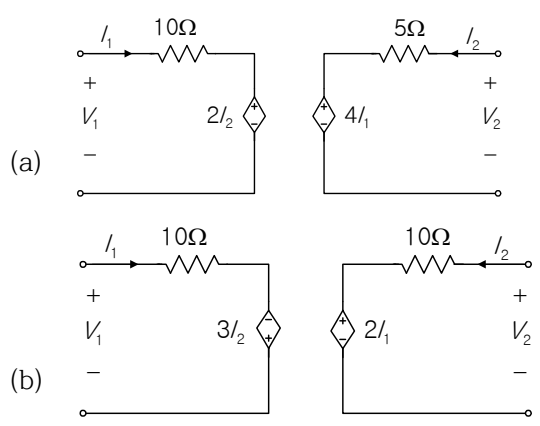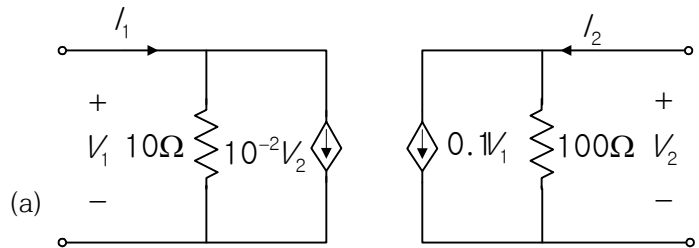번호	답
15.1	<p>(a) <math>z_{11} = 6 + j2 \ [\Omega]</math>, <math>z_{12} = 2 + j2 \ [\Omega]</math>, <math>z_{21} = 2 + j2 \ [\Omega]</math>, <math>z_{22} = 2 - j2 \ [\Omega]</math>  <math>y_{11} = \frac{1}{8} [\text{S}]</math>, <math>y_{21} = -j\frac{1}{8} [\text{S}]</math>, <math>y_{12} = -j\frac{1}{8} [\text{S}]</math>, <math>y_{22} = \frac{1}{8} - j\frac{1}{4} [\text{S}]</math></p> <p>(b) <math>z_{11} = \frac{150}{7} \ [\Omega]</math>, <math>z_{12} = -\frac{130}{7} \ [\Omega]</math>, <math>z_{21} = z_{22} = \frac{10}{21} \ [\Omega]</math>  <math>y_{11} = 25 [m\text{S}]</math>, <math>y_{21} = -25 [m\text{S}]</math>, <math>y_{12} = 0.975 \ [\text{S}]</math>, <math>y_{22} = 4.5 [\text{S}]</math></p> <p>(c) <math>z_{11} = \frac{10}{3} \ [\Omega]</math>, <math>z_{12} = \frac{5}{3} \ [\Omega]</math>, <math>z_{21} = \frac{5}{3} [\Omega]</math>, <math>z_{22} = \frac{10}{3} [\Omega]</math>  <math>y_{11} = \frac{2}{5} [\text{S}]</math>, <math>y_{12} = -\frac{1}{5} [\text{S}]</math>, <math>y_{21} = -\frac{1}{5} [\text{S}]</math>, <math>y_{22} = \frac{1}{5} [\text{S}]</math></p> <p>(d) <math>z_{11} = 5 \ [\Omega]</math>, <math>z_{12} = j5 \ [\Omega]</math>, <math>z_{21} = -j5 [\Omega]</math>, <math>z_{22} = 5(1 - j2) [\Omega]</math>  <math>y_{11} = 0.1 [\text{S}]</math>, <math>y_{21} = j0.1 [\text{S}]</math>, <math>y_{12} = j0.1 \ [\text{S}]</math>, <math>y_{22} = 0.1 [\text{S}]</math></p>
15.2	<p>(a) <math>z_{11} = -10^3 [\Omega]</math>, <math>z_{12} = 10 [\Omega]</math>, <math>z_{21} = -998 [\Omega]</math>, <math>z_{22} = 30 [\Omega]</math></p> <p>(b) <math>z_{11} = \frac{400}{39} [\Omega]</math>, <math>z_{12} = -\frac{20}{39} [\Omega]</math>, <math>z_{21} = -\frac{100}{39} [\Omega]</math>, <math>z_{22} = \frac{200}{39} [\Omega]</math></p>
15.3	 <p>(a)</p> <p>(b)</p>
15.4	$S_{\text{전원}} = 268 + j38.3 [\text{VA}]$
15.5	$z_{11} = 20.3 - j4.8 \ [\Omega]$ , $z_{12} = 2.28 - j0.715 \ [\Omega]$ , $z_{21} = 0.57 - j0.18 \ [\Omega]$ , $z_{22} = 5.54 + j0.142 \ [\Omega]$
15.6	 <p>(a)</p>

<b>15.7</b>	<p>(a) <math>y_{11} = \frac{2}{21} [\text{S}]</math>, <math>y_{12} = -\frac{1}{105} [\text{S}]</math>, <math>y_{21} = \frac{1}{210} [\text{S}]</math>, <math>y_{22} = \frac{1}{105} [\text{S}]</math></p> <p>(b) <math>y_{11} = 0.1 [\text{S}]</math>, <math>y_{12} = -1 [\text{S}]</math>, <math>y_{21} = 10 [\text{S}]</math>, <math>y_{22} = 100 [\text{S}]</math></p>
<b>15.8</b>	
<b>15.9</b>	<p>(a) <math>h_{11} = 0</math>, <math>h_{12} = 1</math>, <math>h_{21} = -1</math>, <math>h_{22} = -j0.2 [\text{S}]</math>  <math>g_{11} = j0.2 [\text{S}]</math>, <math>g_{12} = -1</math>, <math>g_{21} = 1</math>, <math>g_{22} = -j10 [\text{S}]</math></p> <p>(b) <math>h_{11} = 5 - j10 [\text{S}]</math>, <math>h_{21} = 1</math>, <math>h_{12} = -1</math>, <math>h_{22} = -j0.1 [\text{S}]</math>  <math>g_{11} = \frac{1+j}{10} = 0.1 + j0.1 [\text{S}]</math>, <math>g_{12} = 0.5 + j0.5</math>, <math>g_{21} = 0.2 - j0.2</math>, <math>g_{22} = 2.5 + j2.5 [\text{S}]</math></p> <p>(c) <math>h_{11} = \frac{80}{7} [\text{S}]</math>, <math>h_{12} = 0</math>, <math>h_{21} = \frac{1}{7}</math>, <math>h_{22} = 0.1 [\text{S}]</math>  <math>g_{11} = \frac{7}{80} [\text{S}]</math>, <math>g_{12} = 0</math>, <math>g_{21} = \frac{1}{8}</math>, <math>g_{22} = 10 [\text{S}]</math></p> <p>(d) <math>h_{11} = 6(2-j) [\text{S}]</math>, <math>h_{12} = 1.2 + j0.4</math>, <math>h_{21} = -1.2 - j0.4</math>, <math>h_{22} = \left( \frac{1}{75} - j\frac{11}{150} \right) [\text{S}]</math>  <math>g_{11} = \frac{2-j11}{150} [\text{S}]</math>, <math>g_{21} = 1.2 + j0.4</math>, <math>g_{12} = -1.2 - j0.4</math>, <math>g_{22} = 12 - j6 [\text{S}]</math></p>
<b>15.10</b>	

15.11	
15.12	$R_{in} = -\frac{38}{3} [k\Omega]$
15.13	$V_2 = \frac{20}{7} [V]$
15.14	<p>(a) <math>A = \frac{s+1}{s}</math>, <math>B = 1</math>, <math>C = \frac{s^2+s+1}{s}</math>, <math>D = \frac{1}{1+s}</math></p> <p><math>a = s+1</math>, <math>b = 1</math>, <math>c = \frac{s^2+s+1}{s^2+s}</math>, <math>d = \frac{s+1}{s}</math></p> <p>(b) <math>A = \frac{1}{4}</math>, <math>B = \frac{3}{2}</math>, <math>C = -\frac{1}{4}</math>, <math>D = \frac{1}{2}</math>     <math>a = 1</math>, <math>b = 3</math>, <math>c = -0.5</math>, <math>d = 0.5</math></p>
15.15	<p>(a) <math>y_{11} = \frac{5}{52} [\Omega]</math>, <math>y_{12} = \frac{1}{52} [\Omega]</math>, <math>y_{21} = -\frac{1}{52} [\Omega]</math>, <math>y_{22} = \frac{5}{52} [\Omega]</math></p> <p>(b) <math>h_{11} = 10.4 [\Omega]</math>, <math>h_{12} = -0.2</math>, <math>h_{21} = -0.2</math>, <math>h_{22} = 0.1 [\Omega]</math></p> <p>(c) <math>A = 5</math>, <math>C = 0.5 [\Omega]</math>, <math>B = -52 [\Omega]</math>, <math>D = 5</math></p>
15.16	<p>(a) <math>z_{11} = 2010 [\Omega]</math>, <math>z_{12} = -20 [\Omega]</math>, <math>z_{21} = -100 [\Omega]</math>, <math>z_{22} = 1 [\Omega]</math></p> <p>(b) <math>y_{11} = 0.1 [\Omega]</math>, <math>y_{12} = 2 [\Omega]</math>, <math>y_{21} = 10 [\Omega]</math>, <math>y_{22} = 201 [\Omega]</math></p> <p>(c) <math>g_{11} = \frac{1}{2010} [\Omega]</math>, <math>g_{12} = \frac{2}{201}</math>, <math>g_{21} = \frac{10}{9}</math>, <math>g_{22} = \frac{1}{201} [\Omega]</math></p>
15.17	$\frac{V_o}{V_s} = \frac{30}{89}$
15.18	$g_{11} = 0.043 [\Omega]$ , $g_{12} = -0.151$ , $g_{21} = 0.173$ , $g_{22} = -0.938 [\Omega]$
15.19	$g_{11} = 84.0 [m\Omega]$ , $g_{12} = -0.071$ , $g_{21} = 0.071$ , $g_{22} = 0.709 [\Omega]$
15.20	<p>(a) <math>z_{11} = 200 [\Omega]</math>, <math>z_{12} = z_{21} = 100 [\Omega]</math>, <math>z_{22} = 200 [\Omega]</math></p> <p>(b) </p>

	(c) $\frac{V_o}{V_s} = -0.2$
<b>15.21</b>	$h_{11} = 5[\Omega], \quad h_{12} = h_{21} = 0, \quad h_{22} = 0.2[\text{S}]$
<b>15.22</b>	$A = \frac{s^3 + s^2 + 2s + 1}{s}, \quad B = \frac{2s^3 + 2s^2 + 3s + 1}{s},$ $C = \frac{s^4 + s^3 + 3s^2 + 2s + 1}{s}, \quad D = \frac{2s^4 + 2s^3 + 5s^2 + 3s + 1}{s}$